GEE 1106- Basic Electrical and Electronics Engineering

Module –IV Assignment Questions

1. With neat diagrams, explain the construction, operation and VI characteristics of a PN junction diode.
2. With neat diagrams, explain the construction, operation and VI characteristics of a Zener diode.
3. Explain the operation of a Zener diode as a voltage regulator with load line analysis.
4. Explain Half wave rectifier and full-wave rectifier (center-tap / bridge) with circuit diagram and waveforms.
5. Explain the working of types of clippers and clampers with neat circuit diagram.
6. Explain diode protection circuits against overvoltage and overcurrent.
7. Explain the construction and working of an LED with IV characteristics.